

Name: \_\_\_\_\_Servando\_Olvera\_\_\_\_\_ ID# \_\_\_\_\_1001909287\_\_\_\_\_

Date Submitted: \_\_\_\_\_04-18-2024\_\_\_\_\_ Time Submitted \_\_\_\_\_9:00\_pm\_\_\_\_\_

CSE 3341 Digital Logic Design II

CSE 5357 Advanced Digital Logic Design

Spring Semester 2024

**Lab 6 – Keypad Encoder and Scanner**

**100 points**

Due Date – May 18, 2024, 11:59 PM

Submit on Canvas Assignments

# DESIGN REQUIREMENTS

## ***PURPOSE/OUTCOMES***

To design, implement using the DE10-Lite + KeyPad + FlipBoard + HexBoard a keypad scanner and encoder to display keystrokes on a multiplexed seven-segment display. By successfully completing this lab you will be able to use the KeyPad and HexBoard for input and output units for the term project.

## ***BACKGROUND***


A basic calculator can be partitioned in to four functional units. The arithmetic unit (AU) receives two eight-bit operands, with the left-most bit being a sign-bit, encoded in two's complement and produces an output in two's complement. For the four-function term-project calculator, data will be entered in hexadecimal on the KeyPad and displayed in hexadecimal on the HexBoard. Hence, the KeyPad must be configured to output key strokes in hexadecimal characters. Note, the KeyPad (4x4 keypad) must be plugged in to the Arduino port on the DE 10-Lite.

## ***DESIGN REQUIREMENTS***


Your assignment is to configure and test the KeyPad Scanner and Encoder to capture four key strokes and display the hex code on the HexBoard.

1. Implement the BCD KeyPad Scanner and Encoder and display the outputs on the HexBoard.
2. Demonstrate your implementation with an appropriate test.
3. Modify the code to capture hexadecimal characters.
4. Implement the HEX KeyPad Scanner and Encoder and display the outputs on the HexBoard.
5. Demonstrate your implementation with an appropriate test.

## ORGANIZATION DIAGRAM

 

## HIRERARCHY DIAGRAM

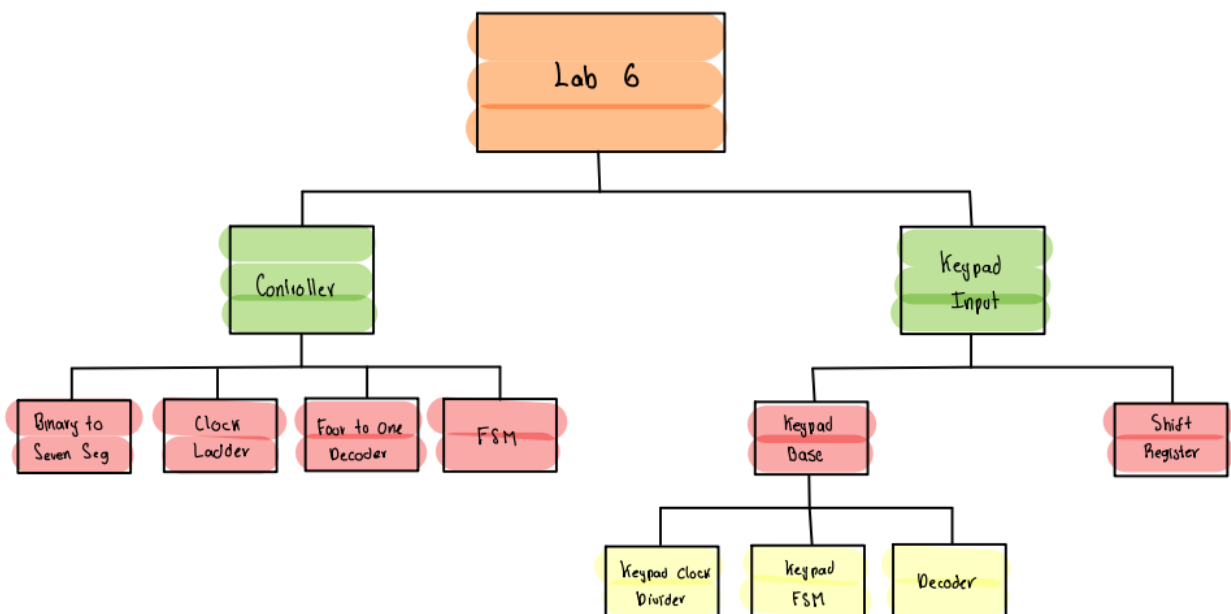

# SYSTEM-VERILOG CODE

## Part Top Module

```
module Lab6
(
    input CLK, CLR, BASE,
    input [3:0] ROW,
    output logic [3:0] COL,
    output logic [0:6] HEX,
    output logic [3:0] CAT
);
    logic [15:0] OUT;

    keypad_input INPUT
    (
        .clk(CLK),
        .reset(CLR),
        .row(ROW),
        .BASE(BASE),
        .col(COL),
        .out(OUT)
    );

    Controller Mux // Display Stuff
    (
        .CLK(CLK),
        .CLEAR(CLR),
        .MODE(1'b1),
        .D0(OUT[3:0]),
        .D1(OUT[7:4]),
        .D2(OUT[11:8]),
        .D3(OUT[15:12]),
        .CAT(CAT),
        .HEX(HEX)
    );
endmodule
```

## Keypad Input

```
module keypad_input #( parameter DIGITS = 4)
(
    input clk,
    input reset,
    input [3:0] row,
    input BASE,
    output [3:0] col,
    output [(DIGITS*4)-1:0] out,
    // Debug
    output logic [3:0] value,
    output logic trig
);
    keypad_base keypad_base
    (
        .clk(clk),
        .row(row),
        .BASE(BASE),
        .col(col),
        .value(value),
        .valid(trig)
    );

    shift_reg #(.COUNT(DIGITS)) shift_reg
    (
        .trig(trig),
        .in(value),
        .out(out),
        .reset(reset)
    );
endmodule
```

## Keypad Base Module

```
module keypad_base // Depends: clock_div, keypad_fsm, keypad_decoder
(
    input clk,
    input [3:0] row,
    input BASE,
    output [3:0] col,
    output [3:0] value,
    output valid,
    // Debug
    output logic slow_clock,
    output logic sense,
    output logic valid_digit,
    output logic [3:0] inv_row
);
    assign inv_row = ~row;

    clock_div #(.DIV(100000)) keypad_clock_divider
    (
        .clk(clk),
        .clk_out(slow_clock)
    );

    keypad_fsm keypad_fsm
    (
        .clk(slow_clock),
        .row(inv_row),
        .col(col),
        .sense(sense)
    );

    keypad_decoder #(.BASE(10)) keypad_key_decoder
    (
        .row(inv_row),
        .col(col),
        .base(BASE),
        .value(value),
        .valid(valid_digit)
    );

    assign valid = valid_digit && sense;
endmodule
```

## Clock Divider Module

```
module clock_div #(parameter WIDTH = 32, parameter DIV = 50) // Defaults to 1MHz
(
    input clk, reset,
    output logic clk_out
);
    logic [WIDTH-1:0] r_reg;
    logic [WIDTH-1:0] r_next;
    logic clk_track;

    always @(posedge clk or posedge reset) begin
        if (reset) begin
            r_reg <= 0;
            clk_track <= 1'b0;
        end
        else if (r_next == DIV) begin
            r_reg <= 0;
            clk_track <= ~clk_track;
        end
        else
            r_reg <= r_next;
        end

        assign r_next = r_reg+1;
        assign clk_out = clk_track;
    endmodule
```

## Keypad FSM Module

```

module keypad_fsm
(
    input clk,
    input [3:0] row,
    output logic [3:0] col,
    output logic sense,
    // Debug
    output logic [3:0] state,
    output trig
);
    assign trig = row[0] || row[1] || row[2] || row[3];
    assign sense = state == 10;

    always @ (posedge clk) begin
        case (state)
            0: begin col = 4'b1111; state = 1; end
            1: if (trig) begin state = 2; end
            2: begin col = 4'b0001; state = 3; end
            3: if (trig) begin state = 10; end else begin state = 4; end
            4: begin col = 4'b0010; state = 5; end
            5: if (trig) begin state = 10; end else begin state = 6; end
            6: begin col = 4'b0100; state = 7; end
            7: if (trig) begin state = 10; end else begin state = 8; end
            8: begin col = 4'b1000; state = 9; end
            9: if (trig) begin state = 10; end else begin state = 0; end
            10: begin state = 11; end
            11: if (~trig) begin state = 0; end
        endcase
    end
endmodule

```

## Keypad Key Decoder Module

```

module keypad_decoder #(parameter BASE = 10) // Default Base 10 (Options: 10,16)
(
    input [3:0] row,
    input [3:0] col,
    input base, // 0 = 10, 1 = 16
    output logic [3:0] value,
    output logic valid // Optional
);
    always @ (row, col) begin
        if (base == 0) begin
            // 1 2 3 A
            // 4 5 6 B
            // 7 8 9 C
            // E 0 F D
            case ({row, col})
                8'b0001_0001: begin value = 1; valid = 1; end // 1
                8'b0001_0010: begin value = 2; valid = 1; end // 2
                8'b0001_0100: begin value = 3; valid = 1; end // 3
                8'b0001_1000: begin value = 10; valid = 1; end // A
                8'b0010_0001: begin value = 4; valid = 1; end // 4
                8'b0010_0010: begin value = 5; valid = 1; end // 5
                8'b0010_0100: begin value = 6; valid = 1; end // 6
                8'b0010_1000: begin value = 11; valid = 1; end // B
                8'b0100_0001: begin value = 7; valid = 1; end // 7
                8'b0100_0010: begin value = 8; valid = 1; end // 8
                8'b0100_0100: begin value = 9; valid = 1; end // 9
                8'b0100_1000: begin value = 12; valid = 1; end // C
                8'b1000_0001: begin value = 14; valid = 1; end // E
                8'b1000_0010: begin value = 0; valid = 1; end // 0
                8'b1000_0100: begin value = 15; valid = 1; end // F
                8'b1000_1000: begin value = 13; valid = 1; end // D
                default: begin value = 0; valid = 0; end // Misc
            endcase
        end
        else if (base == 1) begin
            // 0 1 2 3
            // 4 5 6 7
            // 8 9 A B
            // C D E F
            case ({row, col})
                8'b0001_0001: begin value = 0; valid = 1; end // 0
                8'b0001_0010: begin value = 1; valid = 1; end // 1
                8'b0001_0100: begin value = 2; valid = 1; end // 2
                8'b0001_1000: begin value = 3; valid = 1; end // 3
                8'b0010_0001: begin value = 4; valid = 1; end // 4
                8'b0010_0010: begin value = 5; valid = 1; end // 5
                8'b0010_0100: begin value = 6; valid = 1; end // 6
                8'b0010_1000: begin value = 7; valid = 1; end // 7
                8'b0100_0001: begin value = 8; valid = 1; end // 8
                8'b0100_0010: begin value = 9; valid = 1; end // 9
                8'b0100_0100: begin value = 10; valid = 1; end // A
                8'b0100_1000: begin value = 11; valid = 1; end // B
                8'b1000_0001: begin value = 12; valid = 1; end // C
                8'b1000_0010: begin value = 13; valid = 1; end // D
                8'b1000_0100: begin value = 14; valid = 1; end // E
                8'b1000_1000: begin value = 15; valid = 1; end // F
                default: begin value = 0; valid = 0; end // Misc
            endcase
        end
        else begin
            value = 0; valid = 0; // Invalid Base
        end
    end
endmodule

```

## Shift Register Module

```
module shift_reg #(parameter COUNT = 4, parameter WIDTH = 4)
(
    input trig, reset, dir, // Left = 0, Right = 1
    input [WIDTH-1:0] in,
    output logic [(COUNT*WIDTH)-1:0] out
);
always @ (posedge trig, negedge reset) begin
    if (~reset)
        out <= 0;
    else begin
        if (dir) begin // 1 = Right
            out <= out >> WIDTH;
            out[(COUNT*WIDTH)-1:((COUNT*WIDTH)-1)-WIDTH] <= in;
        end
        else begin // 0 = Left
            out <= out << WIDTH;
            out[WIDTH-1:0] <= in;
        end
    end
end
endmodule
```

## Controller/MUX Module

```
module Controller
(
    input CLK, CLEAR, MODE,
    input [3:0] D0, D1, D2, D3,
    output logic [3:0] CAT,
    output logic [0:6] HEX
);

    logic [1:0] RA;           // Digit in-code
    logic [3:0] out;          // Active Digit on Hex Display
    logic clk190;

    clk_ladder clock
    (
        .CLK(CLK),
        .clk190(clk190)
    );

    four2one decoder          // Four to one module
    (
        .A(RA),
        .D0(D0),
        .D1(D1),
        .D2(D2),
        .D3(D3),
        .OUTPUT(out)
    );

    FSM digit                 // Finite State Machine
    (                         // Actively updates HEX digit
        .CLK(clk190),
        .CLEAR(CLEAR),
        .SEL(RA),
        .CAT(CAT)
    );

    binary2seven Hex         // Display Numbers
    (
        .BIN(out),
        .MODE(MODE),
        .SEV(HEX)
    );

endmodule
```

### Clock Ladder Module

```
module clk_ladder #(parameter N = 32)
(
    input CLK,
    output logic clk190
);
    logic [N-1:0] ladder;

    always_ff @(negedge CLK)
        ladder <= ladder + 1;

    assign clk190 = ladder[17];    // 50MHz/2^n+1
endmodule
```

### Four to One Decoder Module

```
module four2one
(
    input [1:0] A,
    input [3:0] D0, D1, D2, D3,
    output logic [3:0] OUTPUT
);
    always_comb
    case({A})
        2'b00: OUTPUT = D0;    // 1st digit
        2'b01: OUTPUT = D1;    // 2nd digit
        2'b10: OUTPUT = D2;    // 3rd digit
        2'b11: OUTPUT = D3;    // 4th digit
    endcase
endmodule
```

### Finite State Machine Module

```
module FSM
(
    input CLK, CLEAR,
    output logic [1:0] SEL,
    output logic [3:0] CAT
);
    logic [1:0] state, nextstate;

    always @ (negedge CLK, negedge CLEAR)
        if (CLEAR == 0) state <= 2'b0; else state <= nextstate;

    always @ (state)
    case ({state})
        2'b00: begin nextstate = 2'b01; SEL = 2'b00; CAT = 4'b1000; end    // 1st digit
        2'b01: begin nextstate = 2'b10; SEL = 2'b01; CAT = 4'b0100; end    // 2nd digit
        2'b10: begin nextstate = 2'b11; SEL = 2'b10; CAT = 4'b0010; end    // 3rd digit
        2'b11: begin nextstate = 2'b00; SEL = 2'b11; CAT = 4'b0001; end    // 4th digit
    endcase
endmodule
```



## Four to One Decoder Module


```
module binary2seven
(
    input [3:0] BIN, MODE,
    output logic [0:6] SEV
);
    always_comb
    if(MODE == 1'b1) begin
        case ({BIN[3:0]}) // Active-High
            4'b0000: {SEV[0:6]} = 7'b1111110; //0
            4'b0001: {SEV[0:6]} = 7'b0110000; //1
            4'b0010: {SEV[0:6]} = 7'b1101101; //2
            4'b0011: {SEV[0:6]} = 7'b1111001; //3
            4'b0100: {SEV[0:6]} = 7'b0110011; //4
            4'b0101: {SEV[0:6]} = 7'b1011011; //5
            4'b0110: {SEV[0:6]} = 7'b1011111; //6
            4'b0111: {SEV[0:6]} = 7'b1110000; //7
            4'b1000: {SEV[0:6]} = 7'b1111111; //8
            4'b1001: {SEV[0:6]} = 7'b1110011; //9
            4'b1010: {SEV[0:6]} = 7'b1110111; //A
            4'b1011: {SEV[0:6]} = 7'b0011111; //b
            4'b1100: {SEV[0:6]} = 7'b1001110; //C
            4'b1101: {SEV[0:6]} = 7'b0111101; //d
            4'b1110: {SEV[0:6]} = 7'b1001111; //E
            4'b1111: {SEV[0:6]} = 7'b1000111; //F
        endcase
    end else begin
        case ({BIN[3:0]}) //Active-Low
            4'b0000: {SEV[0:6]} = 7'b0000001; //0
            4'b0001: {SEV[0:6]} = 7'b1001111; //1
            4'b0010: {SEV[0:6]} = 7'b0010010; //2
            4'b0011: {SEV[0:6]} = 7'b0000110; //3
            4'b0100: {SEV[0:6]} = 7'b1001100; //4
            4'b0101: {SEV[0:6]} = 7'b0100100; //5
            4'b0110: {SEV[0:6]} = 7'b0100000; //6
            4'b0111: {SEV[0:6]} = 7'b0001111; //7
            4'b1000: {SEV[0:6]} = 7'b0000000; //8
            4'b1001: {SEV[0:6]} = 7'b0001100; //9
            4'b1010: {SEV[0:6]} = 7'b0001000; //A
            4'b1011: {SEV[0:6]} = 7'b1100000; //b
            4'b1100: {SEV[0:6]} = 7'b0110001; //C
            4'b1101: {SEV[0:6]} = 7'b1000010; //d
            4'b1110: {SEV[0:6]} = 7'b0110000; //E
            4'b1111: {SEV[0:6]} = 7'b0111000; //F
        endcase
    end
endmodule
```

## PIN ASSIGNMENTS


|    | tatu | From    | To          | Assignment Name | Value    | Enabled |
|----|------|---------|-------------|-----------------|----------|---------|
| 1  | ✓    |         | in- CLR     | Location        | PIN_B8   | Yes     |
| 2  | ✓    |         | out- CAT[0] | Location        | PIN_W8   | Yes     |
| 3  | ✓    |         | out- CAT[1] | Location        | PIN_V8   | Yes     |
| 4  | ✓    |         | out- CAT[2] | Location        | PIN_W9   | Yes     |
| 5  | ✓    |         | out- CAT[3] | Location        | PIN_V9   | Yes     |
| 6  | ✓    |         | out- HEX[0] | Location        | PIN_AA6  | Yes     |
| 7  | ✓    |         | out- HEX[1] | Location        | PIN_Y5   | Yes     |
| 8  | ✓    |         | out- HEX[2] | Location        | PIN_AA5  | Yes     |
| 9  | ✓    |         | out- HEX[3] | Location        | PIN_Y4   | Yes     |
| 10 | ✓    |         | out- HEX[4] | Location        | PIN_AB3  | Yes     |
| 11 | ✓    |         | out- HEX[5] | Location        | PIN_Y3   | Yes     |
| 12 | ✓    |         | out- HEX[6] | Location        | PIN_W7   | Yes     |
| 13 | ✓    |         | in- CLK     | Location        | PIN_P11  | Yes     |
| 14 | ✓    |         | out- COL[0] | Location        | PIN_AA12 | Yes     |
| 15 | ✓    |         | out- COL[1] | Location        | PIN_AA11 | Yes     |
| 16 | ✓    |         | out- COL[2] | Location        | PIN_Y10  | Yes     |
| 17 | ✓    |         | out- COL[3] | Location        | PIN_AB9  | Yes     |
| 18 | ✓    |         | in- ROW[0]  | Location        | PIN_AB8  | Yes     |
| 19 | ✓    |         | in- ROW[1]  | Location        | PIN_AB7  | Yes     |
| 20 | ✓    |         | in- ROW[2]  | Location        | PIN_AB6  | Yes     |
| 21 | ✓    |         | in- ROW[3]  | Location        | PIN_AB5  | Yes     |
| 22 | ✓    |         | in- BASE    | Location        | PIN_C10  | Yes     |
| 23 |      | <<new>> | <<new>>     | <<new>>         |          |         |

# RTL DIAGRAMS


## Top Module

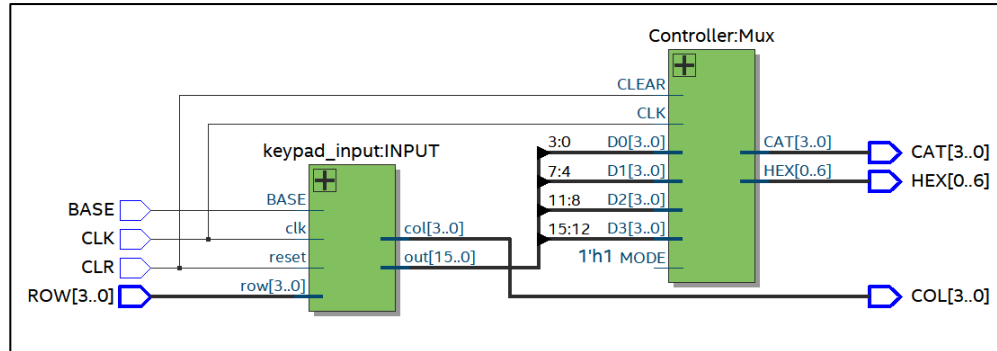


## Keypad Input

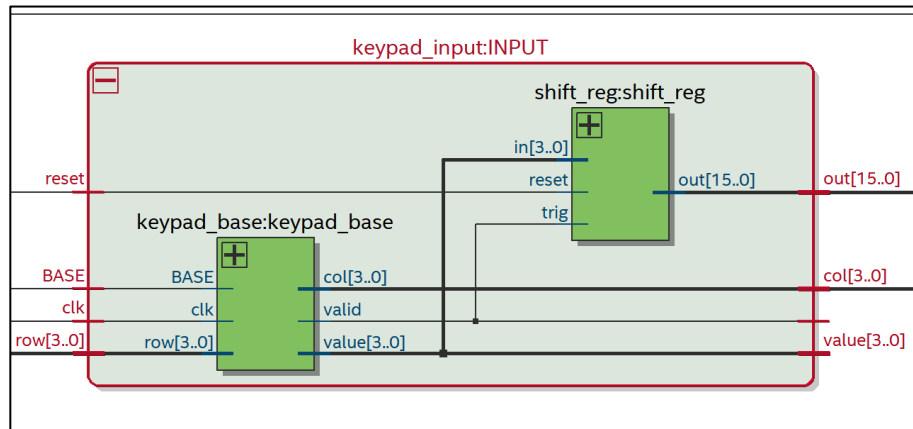


## Keypad Base

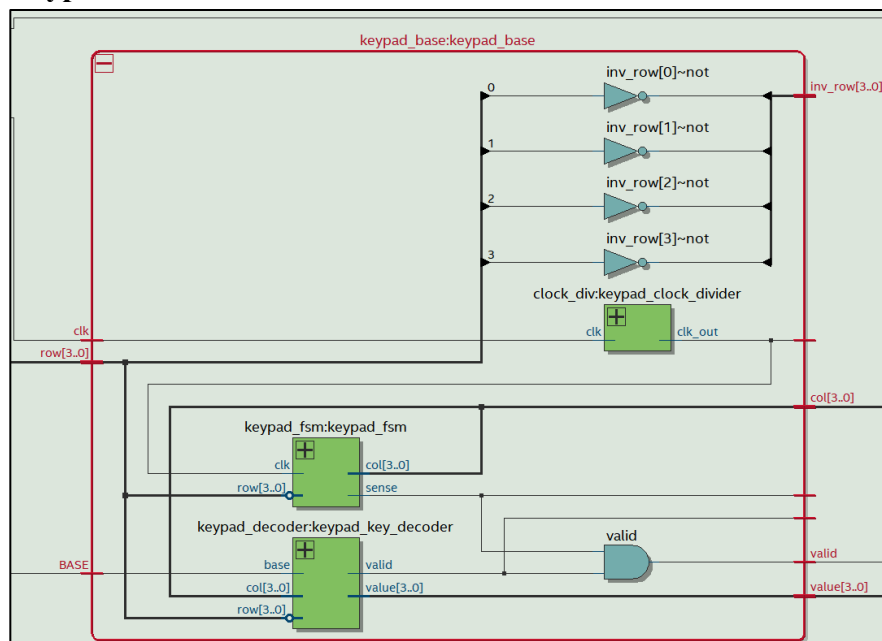


## Clock Divider

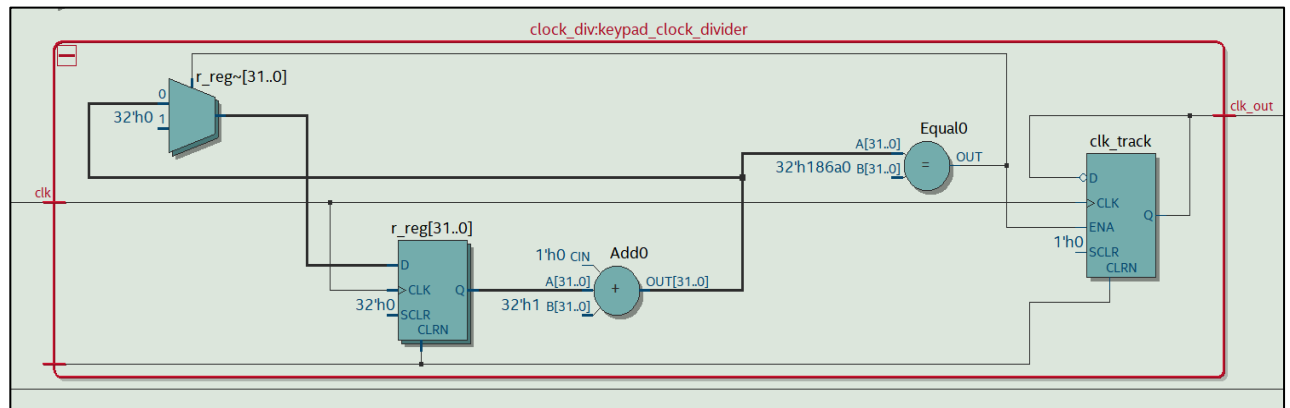


## Keypad Finite State Machine

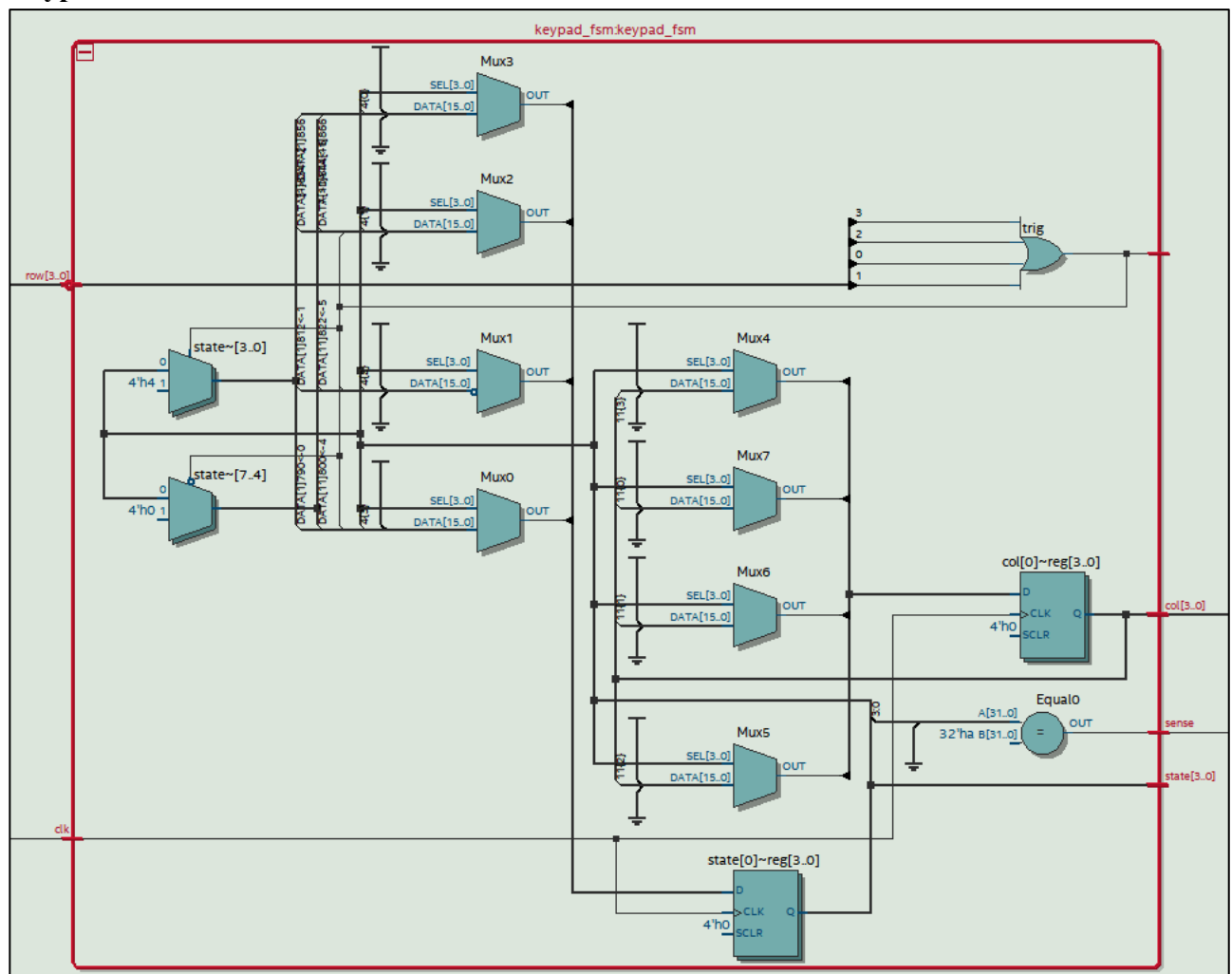


## Keypad Key Decoder

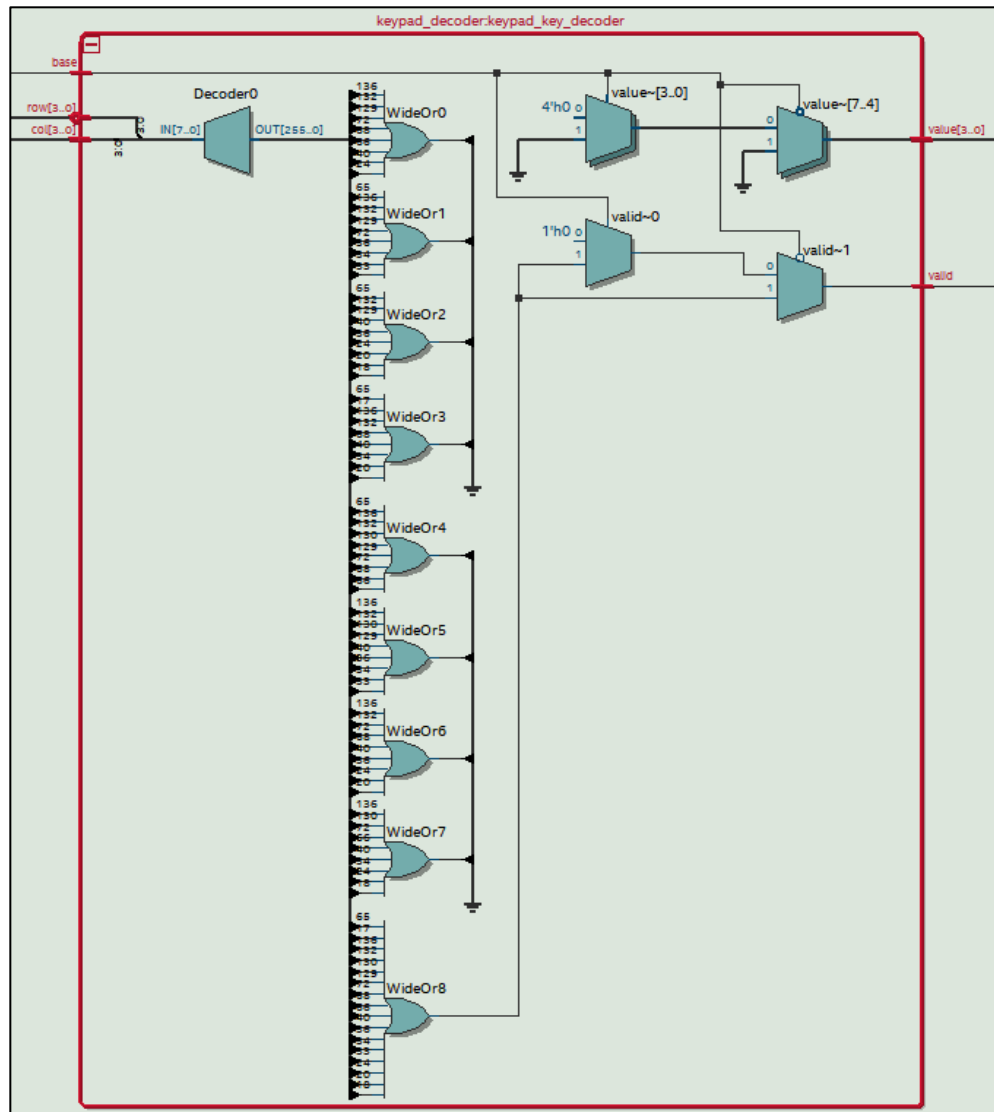


## Shift Register

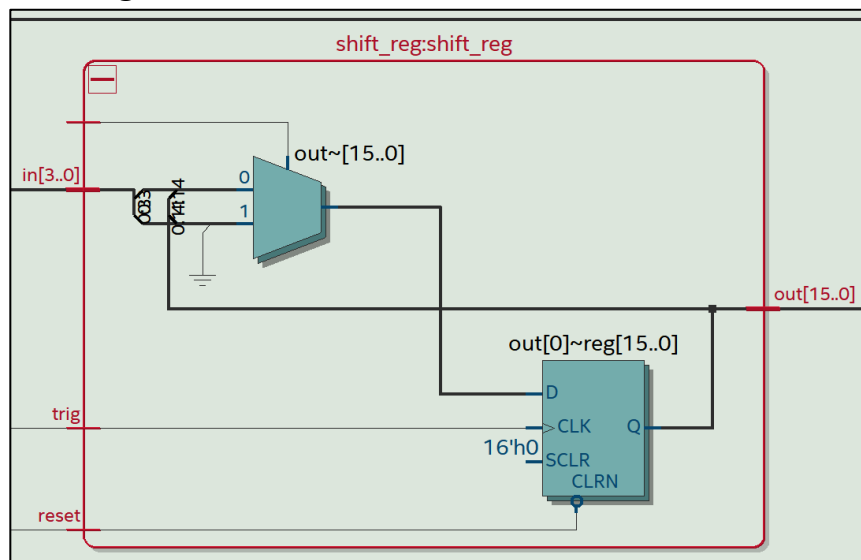


## Controller/MUX

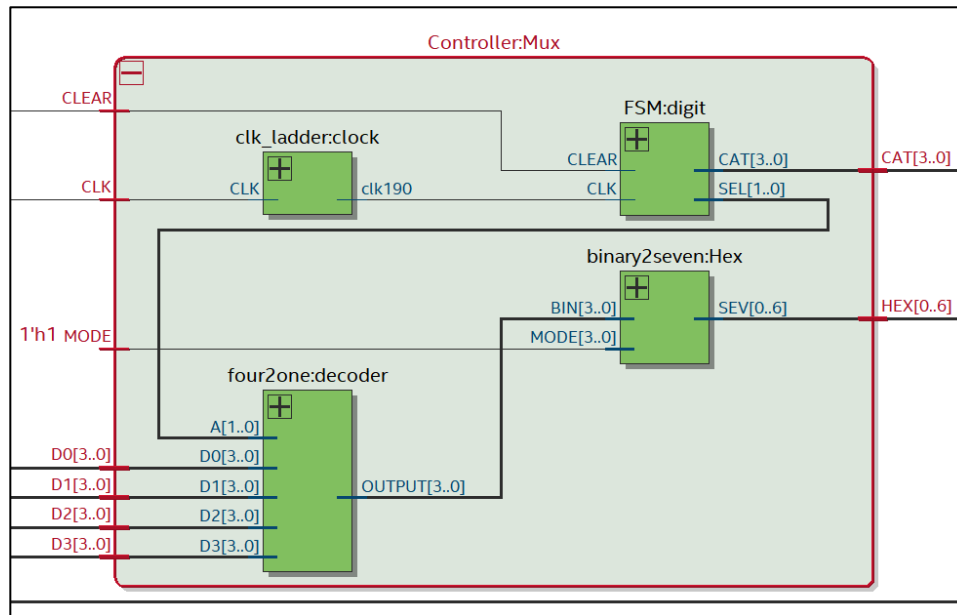


## Four to One Decoder

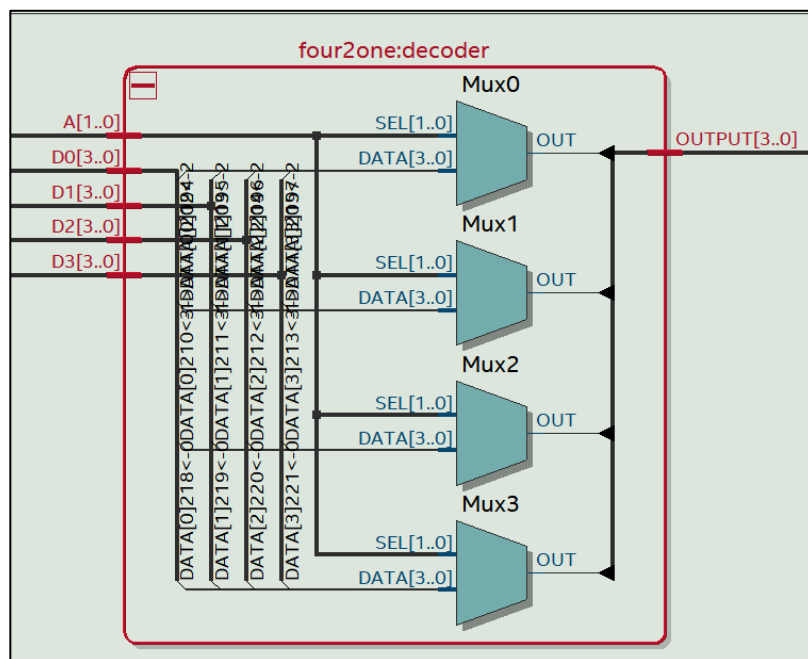


## Clock Ladder

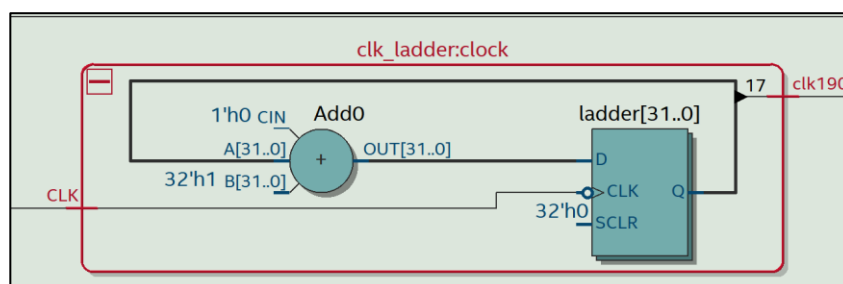


## Finite State Machine

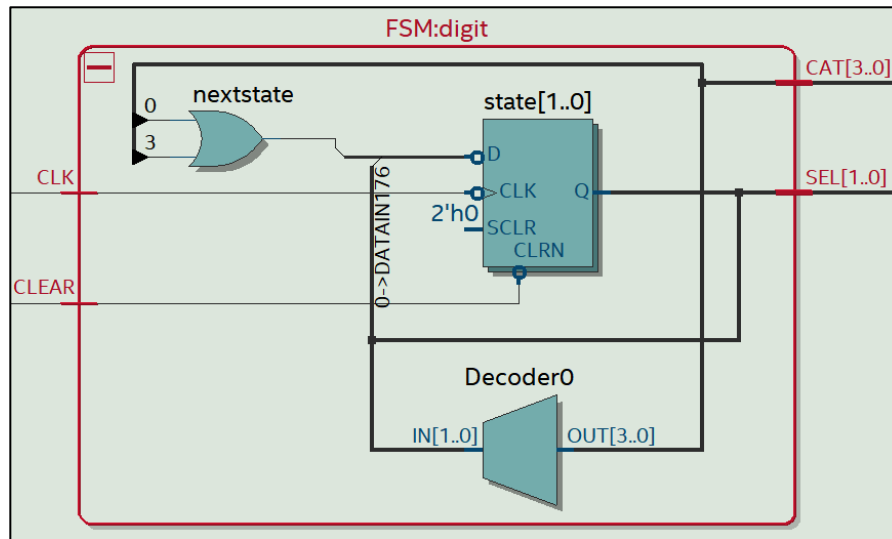

## Binary To Seven Hex Decoder

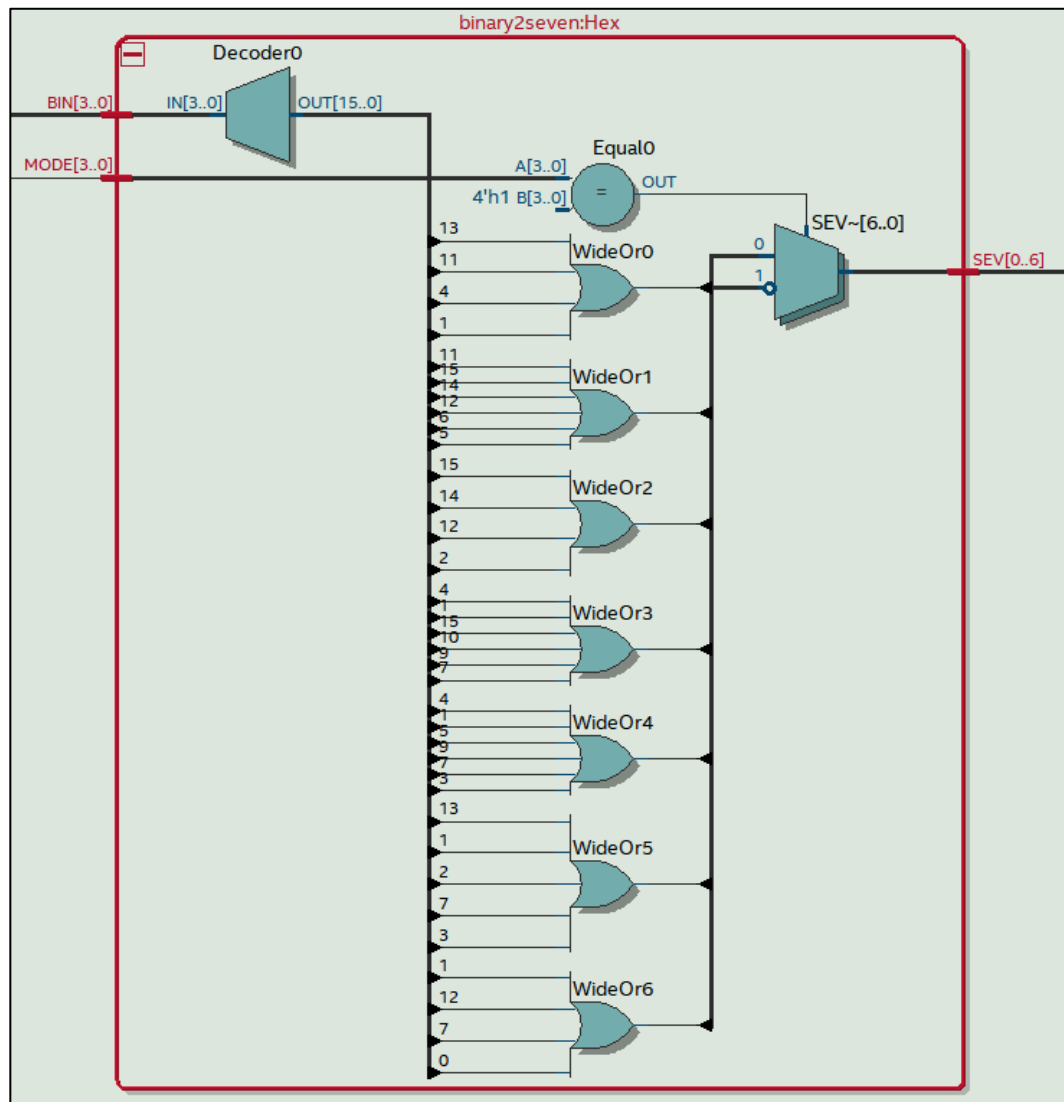

## Compilation Summary

| Flow Summary   |   |
|--|---|
|  <<Filter>> |   |
| Flow Status  | Successful - Tue Apr 16 17:37:33 2024       |
| Quartus Prime Version  | 20.1.1 Build 720 11/11/2020 SJ Lite Edition |
| Revision Name  | Lab6  |
| Top-level Entity Name  | Lab6  |
| Family   | MAX 10                                      |
| Device   | 10M50DAF484C7G                              |
| Timing Models  | Final                                       |
| Total logic elements   | 174 / 49,760 ( < 1 % )                      |
| Total registers  | 83  |
| Total pins   | 22 / 360 ( 6 % )                            |
| Total virtual pins   | 0   |
| Total memory bits  | 0 / 1,677,312 ( 0 % )                       |
| Embedded Multiplier 9-bit elements   | 0 / 288 ( 0 % )                             |
| Total PLLs   | 0 / 4 ( 0 % )                               |
| UFM blocks   | 0 / 1 ( 0 % )                               |
| ADC blocks   | 0 / 2 ( 0 % )                               |

## DEMONSTRATION OF DCB KEYPAD SCANNER

Demoed In person to TA.

## DEMONSTRATION OF HEX KEYPAD SCANNER

Demoed In person to TA.