

CLA4 carry

$$\begin{aligned} C_0 &= C_{in} \\ C_1 &= p_0 C_0 + g_0 \\ C_2 &= p_1 C_1 + g_1 \\ C_3 &= p_2 C_2 + g_2 \\ C_4 &= p_3 C_3 + g_3 \end{aligned}$$

CLA Equations

$$\begin{aligned} S &= A \oplus B \oplus C_{in} \\ C_{out} &= a'b'c_{in} + b'a'c_{in} + ab'c_{in} + abc_{in} \\ &= (a'b + ab')c_{in} + ab(c_{in} + c_{in}') \\ &= (a \oplus b)c_{in} + ab \\ &= pc_{in} + g \\ p &= a \oplus b \\ g &= ab \end{aligned}$$

Clock Ladder

Input Clock Frequency = f_{CLK}


$$\begin{aligned} f_{y0} &= \frac{f_{clk}}{2} \\ f_{y1} &= \frac{f_{clk}}{4} \\ f_{y2} &= \frac{f_{clk}}{8} \\ f_{y3} &= \frac{f_{clk}}{16} \end{aligned} \quad f_{yn} = \frac{f_{clk}}{2^{n+1}}$$

Sync a clock to an async input like a switch can lead to multiple reads per clock pulse, or unpredictable behavior by the switch. Solutions:

- Slow the clock speed to control unit
- Add transition states
- Use edge detection on switch

Overflow creates the wrong sign bit.

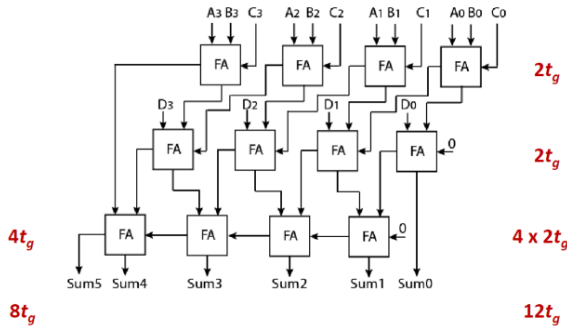1. When adding two (+) numbers that yield a (-) number
 2. When adding two (-) numbers that yield a (+) number
- i.e. $7 + 7 \neq -2$ $-8 + -8 \neq 0$



In a 4x4 keypad scanning algo. Upon pressing any of the buttons on a given row, this one will send a signal to the Keypad Scanner & Encoder. Then columns are scanned. Having both the row and column, the specific button that was pressed can be determined. Code corresponding to button is outputted, along w a signal that tell whether code is ready.

```
module Register #(parameter N=4)
(
    input LOAD, CLR,
    input [N-1:0] ABCD,
    output logic [N-1:0] Q
);
    always_ff @(posedge LOAD, negedge CLR) begin
        if (CLR == 1'b0) Q <= 0;
        else if (LOAD == 1'b1) Q <= ABCD;
    end
endmodule
```

For 4 chained CLAs

$$\text{Add Time} = 4t_g + 4t_g + 4t_g + 4t_g$$

One CLA4: takes $1t_g$ to compute propagate and generate; takes $2t_g$ to compute C_{out} (2 logic gates needed); and computing sum takes $1t_g$

$$1 \text{ CLA4 Add Time} = 4t_g$$

$$[50\text{MHz} \rightarrow 5\text{Hz}] = \left[\frac{50 \times 10^6}{1000} = 50,000\text{Hz} \right] \rightarrow \left[\frac{50,000}{100} = 500\text{Hz} \right] \rightarrow \left[\frac{500}{10} = 50\text{Hz} \right] \rightarrow \left[\frac{50}{10} = 5\text{Hz} \right]$$

* **Data Arrival Time (DAT):** the time it takes for the data to arrive at the destination register input.

- Max
- Min

* **Clock Arrival Time (Tclk):** the time it takes for the clock to arrive at the destination register

- Max
- Min

* **Data Required Time (setup) = Clock Arrival Time – Setup Time**

- Max
- Min

* **Data Required Time (hold): = Clock Arrival Time + Hold Time**

- Max
- Min

* **Setup slack = clock period + minimum data required time – max data arrival time**

Dependent on frequency!

* **Hold slack = minimum data arrival time – max data required time**

NOT dependent on frequency!

* **Max clock frequency**

new period = clock period + |setup slack|

$$T_{MIN} = DAT_{MAX} + \text{Setup Time} - T_{clkMIN}$$

$$F_{MAX} = \frac{1}{T_{min}}$$

* If setup slack < 0, then logic design is rather slow. Fix by increasing the period, or, in other words, decreasing frequency.

```
logic clk1;
```


```
// 2^10 = 1024
// Able to hold 1000
// input CLK = 50 MHz
divideXN #(1000, 10) name // 50*10^6
) // ----- = 50,000
    .CLK(CLK),
    .CLEAR(CLR),
    .OUT(Clk1), // Clk1 = 50,000 kHz
);
```

```
module CLK_Ladder #(parameter N=4)
```

```
(
    input CLK, CLR,
    output logic [N-1:0] ladder
)
    always_ff @(posedge CLK, negedge CLR) begin
        if (CLR == 1'b0)
            ladder <= 0;
        else
            ladder <= ladder + 1'b1;
    end
endmodule
```

```
module Neg_EdgeDetect
```
 
```
(
    input IN, CLK,
    output logic OUT
)
    logic IN_delay
    always_ff @(negedge CLK)
        IN_delay <= in;
    assign out = ~IN & IN_delay
endmodule
```



$$H = AC + AB + AD$$

AB \ C	00	01	11	10
00		1		
01	1	1		
11	1	1	1	1
10		1	1	1

$$H = AC + AB + AD + BC + CD$$

Three Static 1 hazards


$$\begin{aligned} 0111 &\leftrightarrow 1111 \\ 0110 &\leftrightarrow 1110 \\ 0011 &\leftrightarrow 1011 \end{aligned}$$

Multiplexed displays Advantages:

- fewer pin assignments required
- Simpler and shorter code
- easier to implement
- separate Anodes as supposed to single
- less wiring than non-multiplexed
- more efficient

Disadvantages:

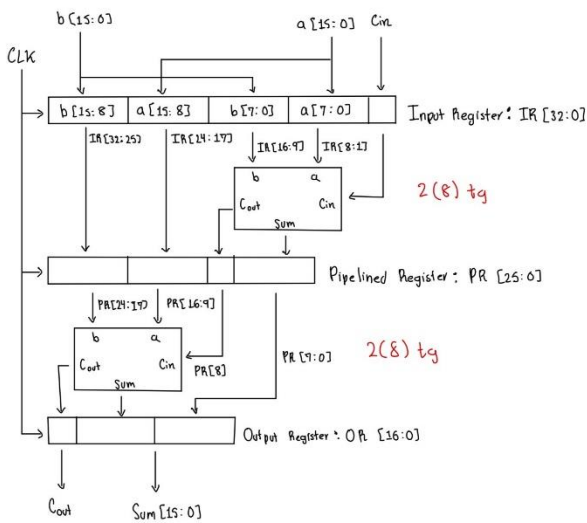- clock rate for cycling thru digits must be set, otherwise flickering
- dimmer than non-multiplexed displays



```

module RCAddSubReg
(
    input AddSub,
    input clock,
    input [3:0] A, B,
    output [3:0] S_out,
    output Cout
);
    logic [3:0] reg_A, reg_B, reg_S;
    logic reg_C;

    logic [4:0] C;
    logic [3:0] S;

    assign C[0] = AddSub;
    assign Cout = reg_C;
    assign S_out = reg_S;

    always_ff @(negedge clock) begin
        reg_A <= A; reg_B <= B; //load input registers
        reg_S <= S; reg_C <= C[4]; //load output registers
    end

    FAbehavSV s0 (reg_A[0], AddSub^reg_B[0], C[0], S[0], C[1]);
    FAbehavSV s1 (reg_A[1], AddSub^reg_B[1], C[1], S[1], C[2]);
    FAbehavSV s2 (reg_A[2], AddSub^reg_B[2], C[2], S[2], C[3]);
    FAbehavSV s3 (reg_A[3], AddSub^reg_B[3], C[3], S[3], C[4]);
endmodule

```

```

module CirBuff
(
    input CLK, CLR,
    output logic [15:0] data2disp,
    output logic [0:63] msg_out
);
    parameter msg = 64'h0123456789ABCDEF;

    always_ff @(negedge CLK, negedge CLR) begin
        if (CLR == 1'b0)
            msg_out <= message;
        else begin
            msg_out [0:59] <= msg_out [4:63];
            msg_out [60:63] <= msg_out [0:3];
        end
    end

    assign data2disp = msg_out [0:15];
endmodule

```

For an n-bit ripple carry adder, the add time is $2 \cdot n \cdot t_g$

```

// Test Bench
timescale 1ns/100ps
module muxTester (output out);
    logic [2:0] count;
    logic muxOut;

    mux UUT (muxOut, count[2], count[1], count[0]);

    initial begin
        $monitor ($time, "a b sel = %b, muxOut = %b", count, muxOut);
        for (count = 0; count != 3'b111; count++)
            #10;
        #10 $finish; // After test is done wait 10 ns
    end
endmodule : muxTester

// Module to be tested
module mux
(output logic f,
input logic a, b, sel);

    and #2 g1 (f1, a, n_sel),
    g2 (f2, b, sel);
    or #2 g3 (f, f1, f2);
    not g4 (n_sel, sel);
endmodule: mux

```